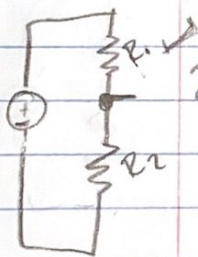


Pre lab 1.2

1a. An ideal voltage meter has infinite internal resistance and should be in parallel with the circuit or device being tested.

b. An ideal current meter has zero internal resistance and should be in series with the circuit or device being tested.



$$2. S_{R_i}^{Req} = R_i \cdot \frac{d}{dR_i} (\log Req)$$

$$R_r = \frac{R_2}{R_1 + R_2}$$

$$S_{R_i}^{R_r} = R_i \cdot \frac{d}{dR_i} (\log R_r)$$

$$S_{R_i}^{R_r} = \frac{R_i}{R_r} \cdot \frac{dR_r}{dR_i}$$

$$\frac{R_1}{R_1 + R_2} \cdot \frac{d}{dR_1} \left(\log \frac{R_2}{R_1 + R_2} \right)$$

$$S_{R_2}^{R_r} = \frac{R_2}{R_1 + R_2} \cdot \frac{dR_r}{dR_2}$$


$$\frac{R_1(R_1 + R_2)}{R_2} \cdot \frac{d}{dR_2} \left(\log \frac{R_2}{R_1 + R_2} \right)$$

$$S_{R_2}^{R_r} = \frac{R_1}{R_2 + R_1}$$

$$S_{R_1}^{R_r} = -\frac{R_1}{R_2 + R_1}$$

→ The total tolerance is the sensitivity of the voltage divider ratio compared to R_1 and the sensitivity compared to R_2 multiplied by 0.05
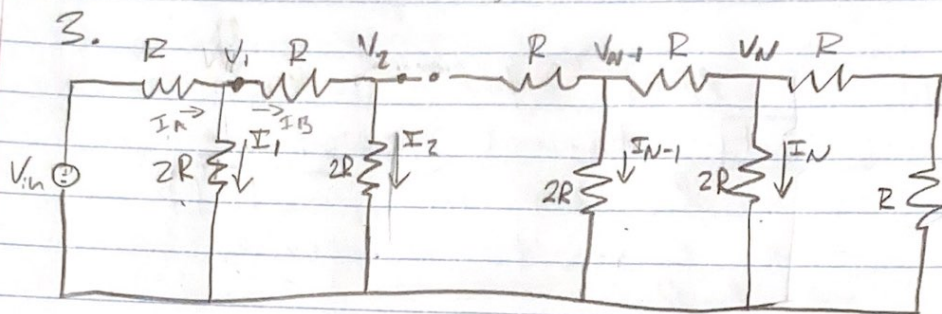
$$T_t = (S_{R_1}^{R_r} + S_{R_2}^{R_r}) \cdot 0.05$$



$$V_1 = V_{in} \left(\frac{R}{R+2R} \right) = V_1 = \frac{1}{2} V_{in}$$

$$V_2 = V_1 \left(\frac{R}{R+2R} \right) = V_2 = \frac{1}{4} V_{in}$$

$$I_1 = V_1 / (2R) = V_{in} / 4R$$

$$I_2 = V_2 / (2R) = \frac{1}{8} V_{in} / R$$



$$I_n = \frac{1}{2^n} V_{in} / R$$

$$2:1$$

$$1:\frac{1}{2}$$

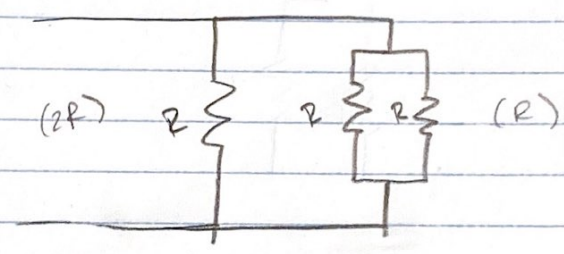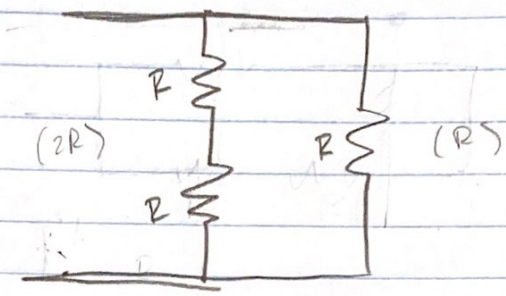4.

$$I_{out} = I_{in} \cdot \frac{R_1 \parallel R_2}{R_2}$$



The second method uses one less resistor in the resistor ladder